

COIMBATORE INSTITUTE OF TECHNOLOGY



CAT-2

REGISTER NO: 1931012

NAME: IVAN HERALD W

CLASS: M.Sc. SOFTWARE SYSTEMS, 4th YEAR

SUBJECT: QUANTUM COMPUTING LABORATORY

SUBJECT CODE: 15MSSL15


AIM

To Construct a 4*1 Multiplexer that consists of 4 parallel inputs and a single output, that is then connected to a D-Flip Flop as a clock input.

SHORT DESCRIPTION


Implementation of this multiplexer and D- Flip Flop is done Using Multiple quantum Gates. The input for this circuit is 4 bits. The following code is a generalized one.

CLASSICAL MULTIPLEXER

 

Selection Lines		Output
s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

CLASSICAL D FLIP FLOP

 

Clock	D	Q	Q'
↓ » 0	0	0	1
↑ » 1	0	0	1
↓ » 0	1	0	1
↑ » 1	1	1	0

CODE

```
from qiskit import QuantumRegister, QuantumCircuit, Aer, execute
from qiskit.visualization import *
```

MULTIPLEXER

```
qc=QuantumCircuit(13,1)
```

```
qc.x(2)
```

```
qc.mct([0,1,5],6)
```

```
qc.x(1)
```

```
qc.mct([0,1,3],7)
```


```
qc.x(0)
qc.mct([0,1,2],8)
```

```
qc.x(1)
qc.mct([0,1,4],9)
```

```
qc.barrier()
qc.ccx(6,7,10)
qc.cx(6,7)
qc.cx(7,10)
```

```
qc.ccx(8,10,11)
qc.cx(10,8)
qc.cx(8,11)
```
 
```
qc.ccx(9,11,12)
qc.cx(11,9)
qc.cx(9,12)
qc.measure(12,0)
qc.barrier()
qc.draw('mpl')
```



```
backend = Aer.get_backend('qasm_simulator')
job = backend.run(qc, shots=1024, memory=True)
output = job.result().get_memory()[0]
print(output)
```

OUTPUT:1

D Flip Flop

```
qc=QuantumCircuit(7,1)
```

```
# qc.x(0)
```

```
# qc.x(1)
```

```
qc.x(4)
```


```
qc.ccx(0,1,2)
```

```
qc.x(2)
```

```

qc.x(1)
qc.ccx(0,1,3)
qc.x(3)
qc.x(1)
qc.ccx(3,4,5)
qc.x(5)
qc.ccx(2,5,4)
qc.x(4)
qc.measure(4,0)
qc.draw('mpl')

```

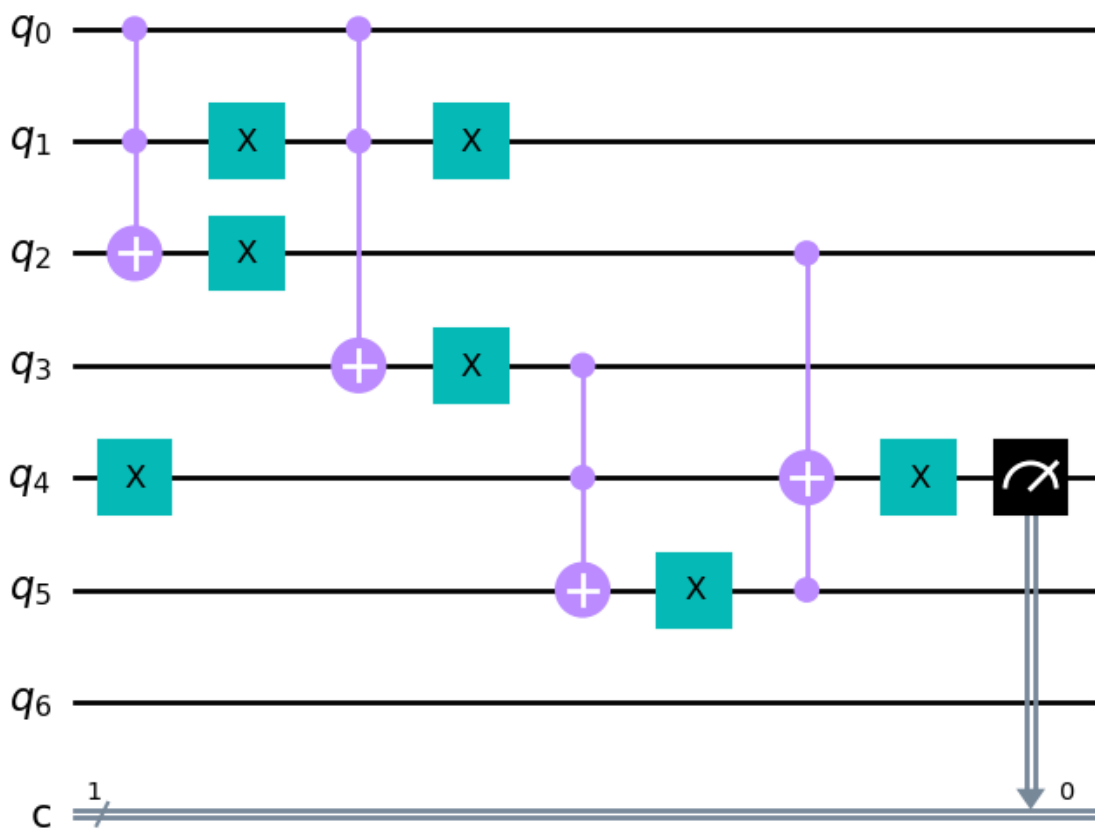

```

backend = Aer.get_backend('qasm_simulator')
job = backend.run(qc, shots=1024, memory=True)

```

```
output = job.result().get_memory()[0]
print(output)
```

OUTPUT: 0

COMPLETE CIRCUIT:

```
qc=QuantumCircuit(18,1)
```

```
# s0 - q0
```

```
# s1 - q1
```

```
# I0 - q2
```

```
# I1 - q3
```

```
# I2 - q4
```

```
# I3 - q5
```

```
# S0 , S1 , I3 - q6
```

```
# S1' , S0 , I1 - q7
```

```
# S1' , S0' , I0 - q8
```

```
# S1 , S0' , I2 - q9
```

```
# multiplexer output - q12
```

```
# D flip flop D - q13
```

```
# Q - q16
```

s0 - 0

s1 - 0

I0 - 1

y - 1 ---> multiplexer output

qc.x(2)

qc.x(13)

qc.mct([0,1,5],6)

qc.x(1)

qc.mct([0,1,3],7)

qc.x(0)

qc.mct([0,1,2],8)

qc.x(1)

qc.mct([0,1,4],9)

qc.barrier()

qc.ccx(6,7,10)

qc.cx(6,7)

qc.cx(7,10)

qc.ccx(8,10,11)

qc.cx(10,8)

qc.cx(8,11)

qc.ccx(9,11,12)

qc.cx(11,9)

qc.cx(9,12)

qc.barrier()

qc.ccx(12,13,14)

qc.x(14)

qc.x(13)

qc.ccx(12,13,15)

qc.x(13)

qc.x(15)

qc.ccx(15,16,17)


qc.x(17)

qc.ccx(14,17,16)

qc.x(16)

qc.measure(16,0)

qc.draw('mpl')

 

```
backend = Aer.get_backend('qasm_simulator')
job = backend.run(qc, shots=1024, memory=True)
output = job.result().get_memory()[0]
print(output)
```

Output: 1

SAMPLE TESTCASES

INPUT:

S0,S1,I0,I1,I2,I3,D,Q

0010000000000100100

OUTPUT:

1

THINGS LEARNED

- To reduce the depth of circuit.
- Tried a new experiment of connecting two different classical circuits and producing a single output.

REFERENCES

- https://www.tutorialspoint.com/digital_circuits/digital_circuits_multiplexers.htm
- <https://www.electronicsforu.com/technology-trends/learn-electronics/flip-flop-rs-jk-t-d>
- <https://arxiv.org/abs/1807.02940#:~:text=Distributing%20entangled%20pairs%20is%20a,pair%20of%20remote%20quantum%20memories.>
- https://www.irjmets.com/uploadedfiles/paper//issue_5_may_2022/22088/final/fin_irjmets1651928209.pdf